

Basic Electronics

-ste Kulov

Electricity is the act of moving particles with a negative charge from one place to another. These particles are called electrons:

$$\text{Electron charge } Q_e = -0.16 \times 10^{-18} \text{ C}$$

$C = \text{Coulombs}$

Potential difference is the potential energy required to move 1 Coulomb of charge:

$$PD = \frac{PE}{Q} \Rightarrow \text{Volts} = \frac{\text{Joules}}{\text{Coulombs}}$$

Current is charge in motion:

$$I = \frac{Q}{T} \Rightarrow \text{Amps} = \frac{\text{Coulombs}}{\text{seconds}}$$

Resistance is opposition to current. Heat is generated due to this opposition.

$$R = \text{resistance} \quad \Omega = \text{ohms}$$

Conduction is the opposite (inverse) of resistance

$$G = \text{conductance} \Rightarrow G = \frac{1}{R} \Leftrightarrow R = \frac{1}{G}$$

$$\text{Siemens} = \frac{1}{\text{Ohms}} \quad \text{or} \quad S = \frac{1}{\Omega}$$

$$\text{mhos} = \text{mho} = \frac{1}{\Omega}$$

Conductors (wires) :
 $R \rightarrow 0$

Silver
Copper
Gold
Aluminum

Insulators:
 $R \rightarrow \infty$


Foam
Wood
Plastic
Paper

Semiconductors:
(Periodic Table)

Silicon
Germanium
Carbon

Simplest Circuit

Conventional
vs.
Electron Flow

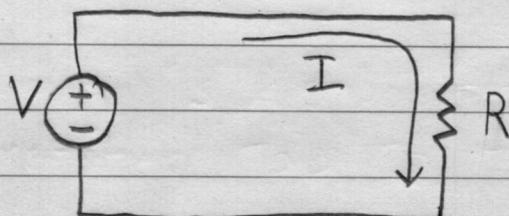

R = load resistance

$R = 0 \Rightarrow$ short circuit

$R = \infty \Rightarrow$ open circuit

"Heavy Load" \Rightarrow low R & high I

"Light Load" \Rightarrow high R & low I

DC: Direct current

Result of constant V

Ex: is a battery

AC: Alternating Current

reverses polarity

usually a sine wave (Hz)


Ex: power outlet in house,

Ohm's Law

$$V = IR$$

volts = amps × ohms

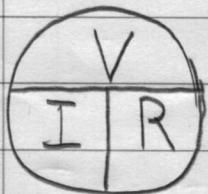
$$I = \frac{V}{R} \quad R = \frac{V}{I}$$



$$9V \begin{array}{c} + \\ \hline - \end{array} I = ? \quad R = 3\Omega \quad I = \frac{9V}{3\Omega} = 3A$$

$$9V \begin{array}{c} + \\ \hline - \end{array} I = 3A \quad R = \frac{9}{3} = 3\Omega$$

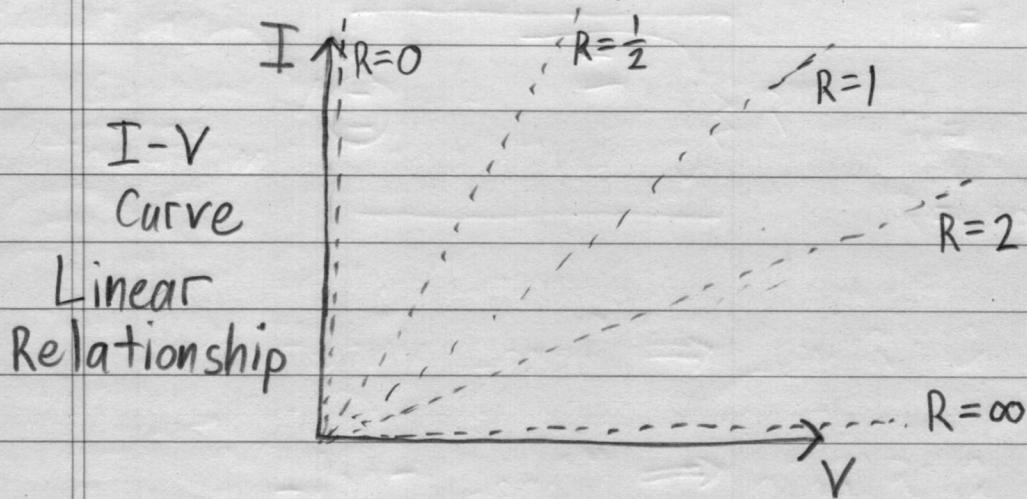
$$? \begin{array}{c} + \\ \hline - \end{array} I = 3A \quad R = 3\Omega \quad V = 3 \cdot 3 = 9V$$



Power: Power = Voltage × Current $P = V \cdot I$

$$P = \frac{V^2}{R} \quad P = I^2 R \quad \text{Watts} = \frac{\text{Joules}}{\text{Second}} \iff W = \frac{J}{S}$$


Series Circuits

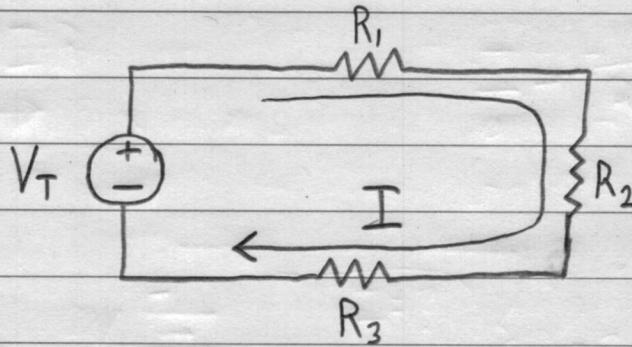

$$R_T = R_1 + R_2 + R_3$$

$$I = \frac{V_T}{R_T}$$

Equivalent Circuit

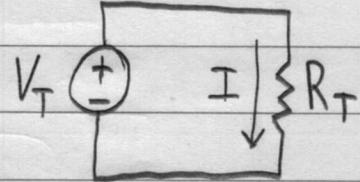

$$V_1 = R_1 \cdot I$$

$$V_2 = R_2 \cdot I$$

$$V_3 = R_3 \cdot I$$

(Voltage Drop)



Kirchoff's Voltage Law : $V_T - V_1 - V_2 - V_3 = 0$

(KVL)

$$\Rightarrow V_T = V_1 + V_2 + V_3$$


$$P_T = P_1 + P_2 + P_3 = V_T \cdot I$$

Series aiding/opposing voltages

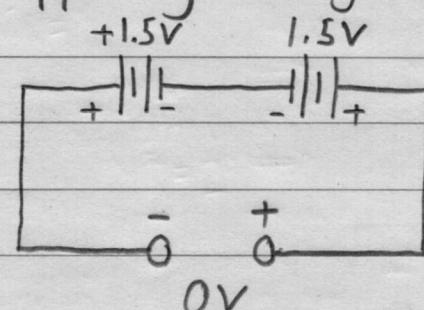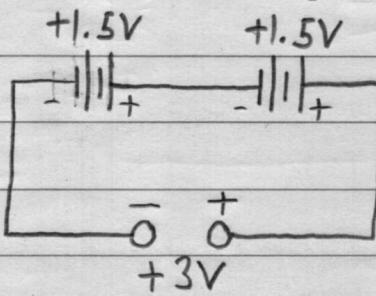


Grounds (common return path)

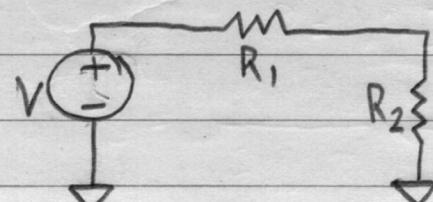Voltages are usually measured with respect to ground
 Ground is considered to be at zero potential



Parallel Circuits

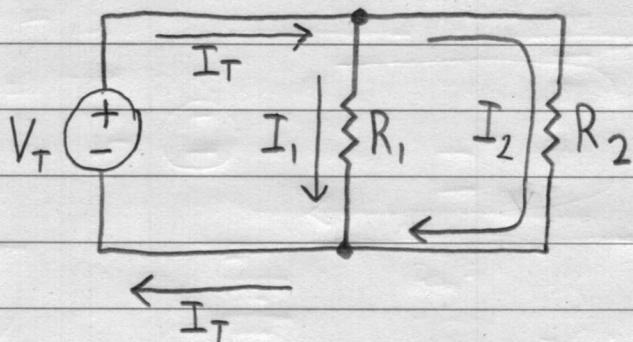


$$V_T = R, I,$$

$$V_T = R_2 I_2$$

Kirchoff's Current Law : $I_T = I_1 + I_2$
(KCL)

$$V_T = R_{eq} I_T$$

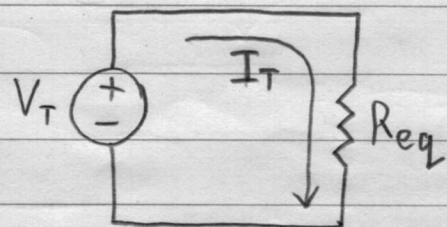

$$\frac{V_T}{R_{eq}} = I_T$$

$$\frac{V_T}{R_{eq}} = I_1 + I_2 = \frac{V_T}{R_1} + \frac{V_T}{R_2}$$

$$V_T \left(\frac{1}{R_{eq}} \right) = V_T \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$





$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

R_{eq} is always less than the lowest separate resistance

Special case when $R_1 = R_2 = R \Rightarrow \frac{R^2}{2R} = \frac{R}{2} = R_{eq}$

$$P_T = P_1 + P_2 = V_T \cdot I_T$$


Circuit Reduction

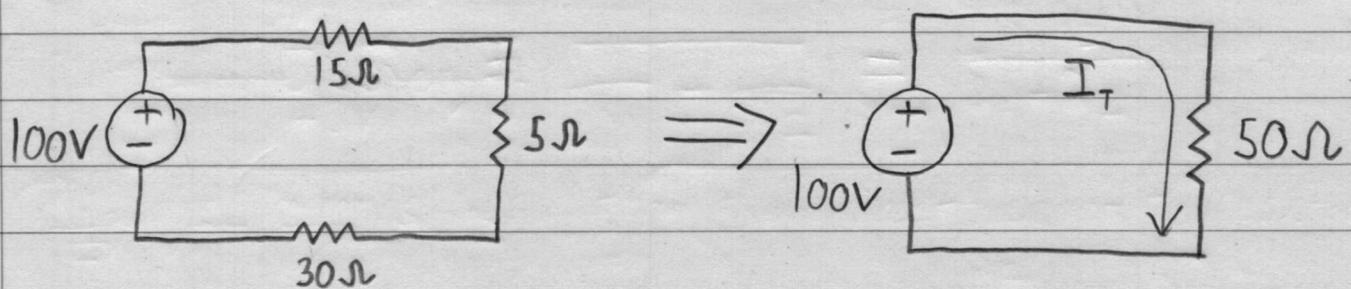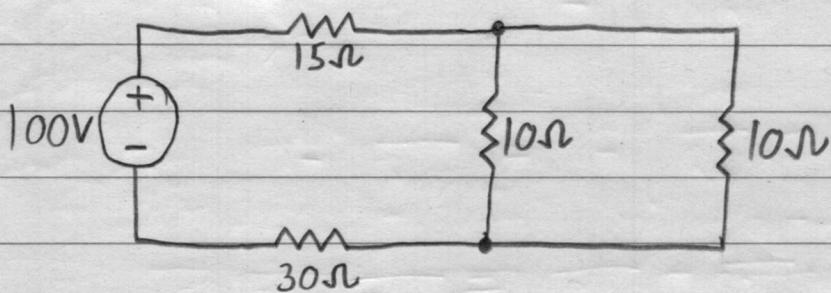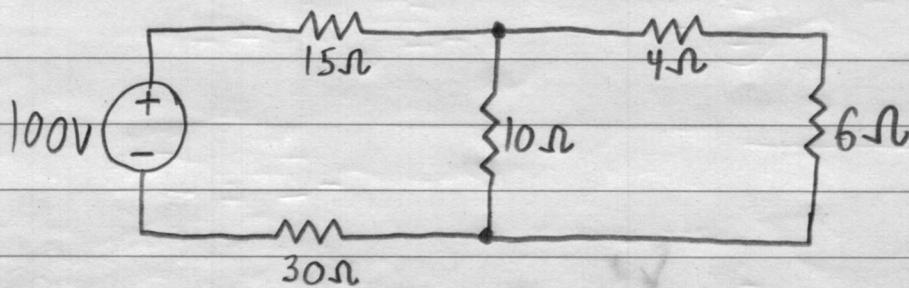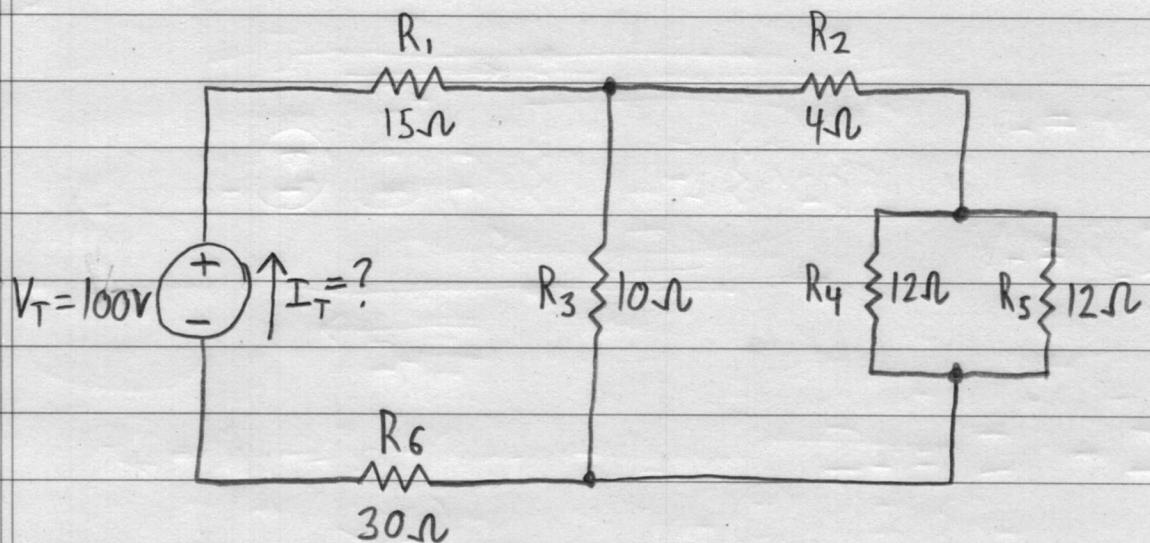

$$I_T = \frac{100V}{50\Omega} = 2A$$

$$P_T = 100V \cdot 2A = 200W$$

Voltage Divider

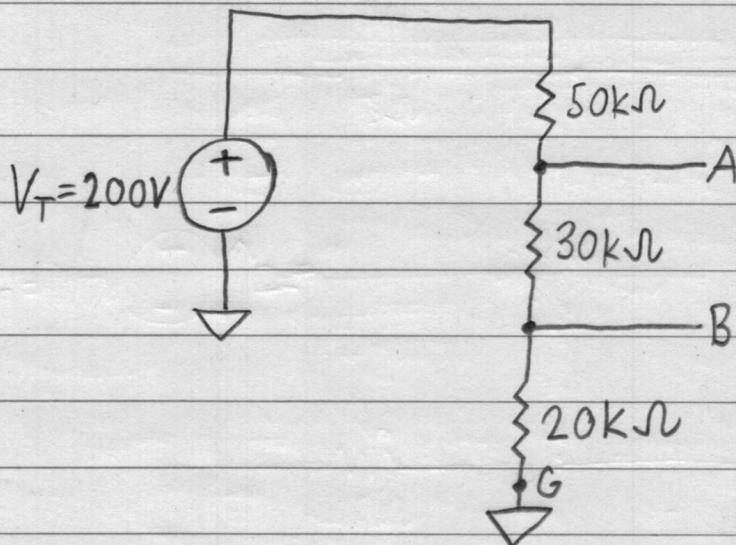

$$V = V_T \cdot \frac{R}{R_T}$$

Series circuit
so $R_T = 50 + 30 + 20 = 100\text{k}\Omega$

A & B are "voltage taps" with respect to G.

$$V_A = V_T \cdot \frac{R_A}{R_T} = 200 \cdot \frac{30+20}{100} = 100\text{V}$$

$$V_B = V_T \cdot \frac{R_B}{R_T} = 200 \cdot \frac{20}{100} = 40\text{V}$$


Current Divider

$$I = I_T \cdot \frac{G}{G_T}$$

$$G_1 = \frac{1}{R_1} = \frac{1}{2} \text{ S}$$

$$G_2 = \frac{1}{R_2} = \frac{1}{4} \text{ S}$$

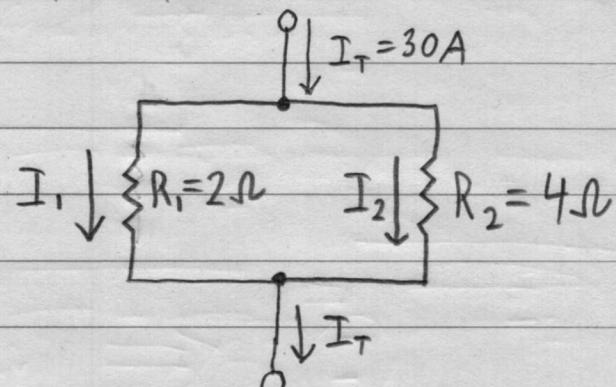
$$G_T = G_1 + G_2 = \frac{1}{2} + \frac{1}{4} = \frac{2}{4} + \frac{1}{4} = \frac{3}{4} \text{ V}$$



$$I_1 = I_T \cdot \frac{G_1}{G_T} = 30 \cdot \frac{\frac{1}{2}}{\frac{3}{4}} = 30 \cdot \frac{1}{2} \cdot \frac{4}{3} = 30 \cdot \frac{2}{3} = 20\text{A}$$

$$I_2 = I_T \cdot \frac{G_2}{G_T} = 30 \cdot \frac{\frac{1}{4}}{\frac{3}{4}} = 30 \cdot \frac{1}{4} \cdot \frac{4}{3} = 30 \cdot \frac{1}{3} = 10\text{A}$$

Branch Currents (straight KVL/KCL)

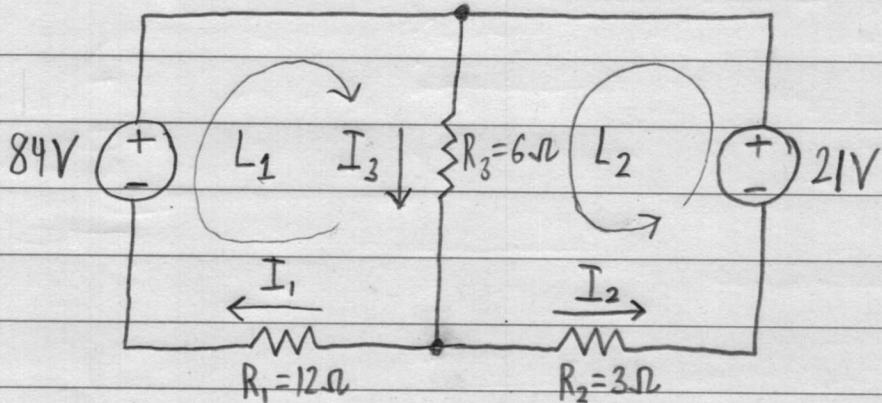

KVL

$$L_1: 84 - V_{R_3} - V_{R_1} = 0 \Rightarrow 84 - I_3 R_3 - I_1 R_1 = 0 \\ 84 - 6I_3 - 12I_1 = 0$$

$$L_2: 21 - V_{R_3} - V_{R_2} = 0 \Rightarrow 21 - I_3 R_3 - I_2 R_2 = 0 \\ 21 - 6I_3 - 3I_2 = 0$$

KCL

$$I_3 = I_1 + I_2 \xrightarrow{L_1} 84 - 6(I_1 + I_2) - 12I_1 = 0 \\ 84 - 6I_1 - 6I_2 - 12I_1 = 0 \\ 84 - 18I_1 - 6I_2 = 0 \\ 18I_1 + 6I_2 = 84 \\ 3I_1 + I_2 = 14$$

$$21 - 6(I_1 + I_2) - 3I_2 = 0$$

$$3I_1 + I_2 = 14$$

$$21 - 6I_1 - 6I_2 - 3I_2 = 0$$

$$2I_1 + 3I_2 = 7$$

$$21 - 6I_1 - 9I_2 = 0$$

$$6I_1 + 9I_2 = 21$$

$$-9I_1 - 3I_2 = -42$$

$$2I_1 + 3I_2 = 7$$

$$2I_1 + 3I_2 = 7$$

$$-7I_1 = -35$$

$$I_1 = 5A$$

$$I_2 = -1A \quad I_3 = 5 - 1 = 4A$$

(Flip Arrow)

$$V_{R1} = I_1 R_1 = 5 \cdot 12 = 60V$$

$$V_{R2} = I_2 R_2 = 1 \cdot 3 = 3V$$

$$V_{R3} = I_3 R_3 = 4 \cdot 6 = 24V$$

$$L1: 84 - 60 - 24 = 0V \quad \checkmark$$

$$L2: 21 + 3 - 24 = 0V \quad \checkmark$$

Node Voltage

$$I_1 + I_2 = I_3$$

$$\Rightarrow \frac{V_{R1}}{R_1} + \frac{V_{R2}}{R_2} = \frac{V_N}{R_3}$$

$$\Rightarrow \frac{V_{R1}}{12} + \frac{V_{R2}}{3} = \frac{V_N}{6}$$

$$84 - V_{R1} - V_N = 0 \Rightarrow V_{R1} = 84 - V_N$$

$$21 - V_{R2} - V_N = 0 \Rightarrow V_{R2} = 21 - V_N$$

$$\frac{84 - V_N}{12} + \frac{21 - V_N}{3} = \frac{V_N}{6}$$

$$84 - V_N + 4(21 - V_N) = 2V_N$$

$$84 - V_N + 84 - 4V_N = 2V_N$$


$$168 - 5V_N = 2V_N$$

$$168 = 7V_N \Rightarrow V_N = 24$$

$$V_{R1} = 84 - V_N \Rightarrow V_{R1} = 84 - 24 = 60V$$

$$V_{R2} = 21 - V_N \Rightarrow V_{R2} = 21 - 24 = -3V \quad (\text{Flip Arrow})$$

Mesh Currents

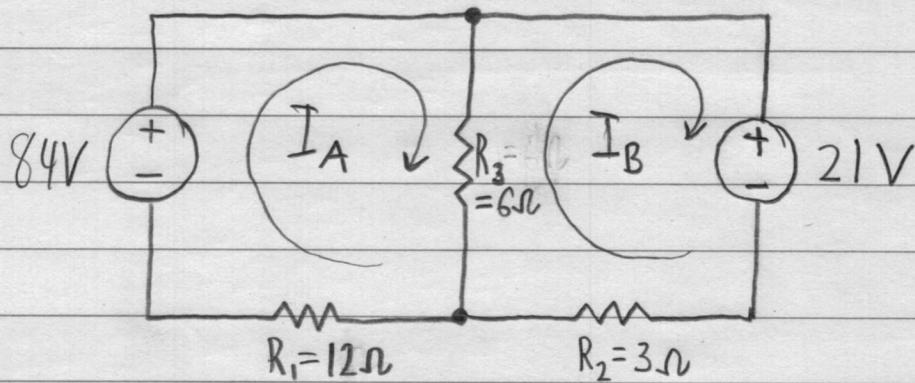

(pick a direction and be consistent) → Clockwise

$$L_A: 84 - 6I_A - 12I_A + 6I_B = 0$$

$$84 - 18I_A + 6I_B = 0$$

$$18I_A - 6I_B = 84$$

$$3I_A - I_B = 14$$

$$3I_A - I_B = 14$$

$$2I_A - 3I_B = 7$$

$$L_B: -21 - 3I_B - 6I_B + 6I_A = 0$$

$$-21 - 9I_B + 6I_A = 0$$

$$6I_A - 9I_B = 21$$

$$2I_A - 3I_B = 21$$

$$-9I_A + 3I_B = -42$$

$$I_{R1} = I_A = 5A$$

$$2I_A - 3I_B = 7$$

$$-7I_A = -35$$

$$I_A = 5A$$

$$I_{R2} = I_B = 1A$$

$$I_{R3} = I_A - I_B = 5 - 1 = 4A$$







$$2 \cdot 5 - 3I_B = 7$$


$$-3I_B = -3$$

$$I_B = 1A$$

Superposition (Linearity)

LTI = Linear Time Invariant

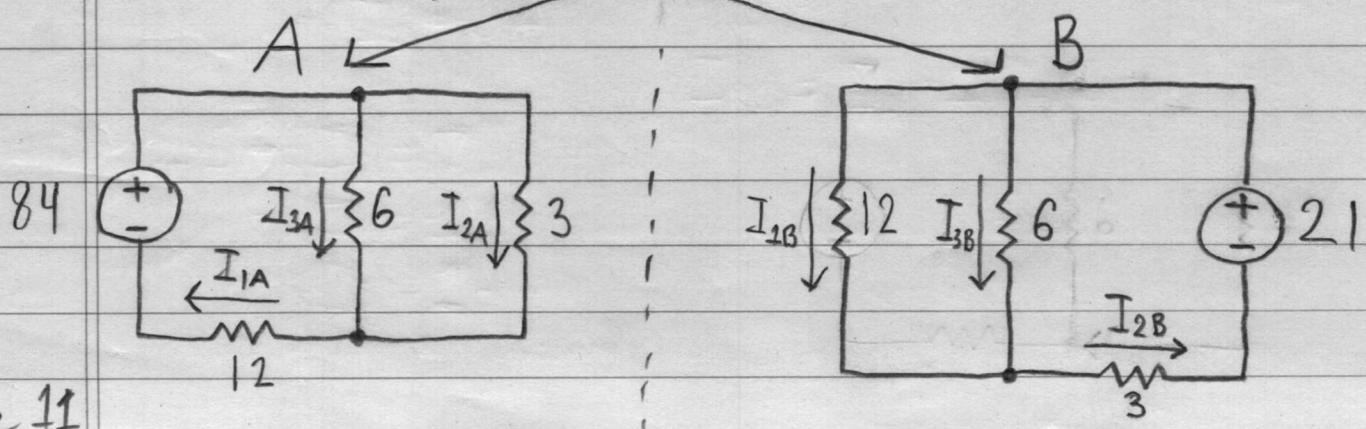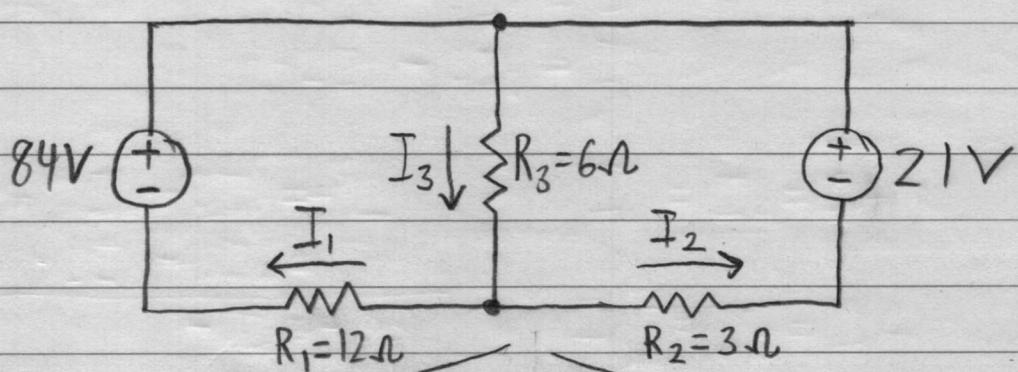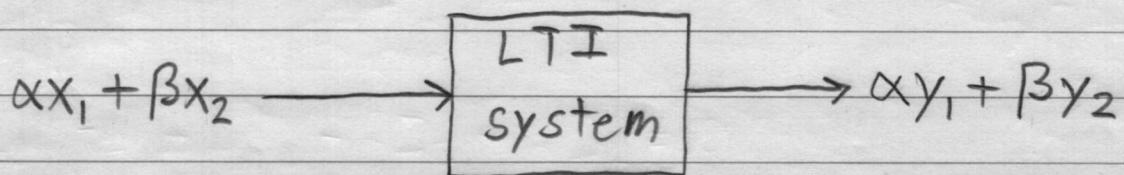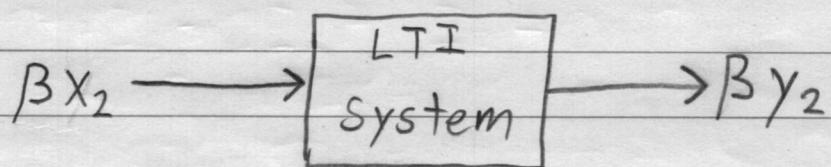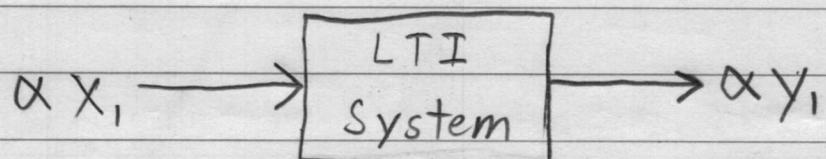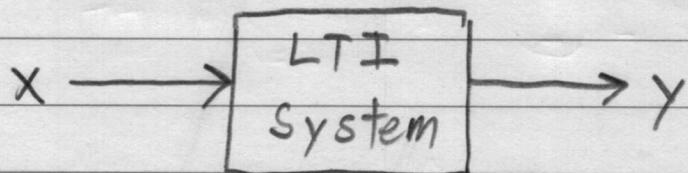

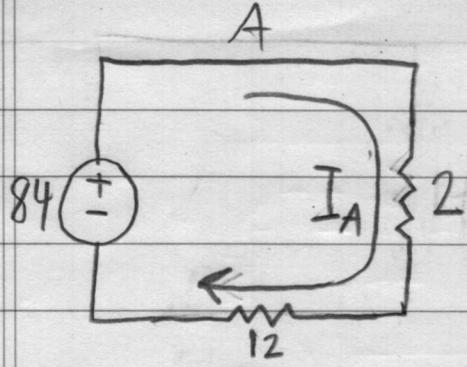

$$I_A = \frac{84}{12+2} = 6$$


$$V_a = 2 \cdot 6 = 12$$

~~$$V_b = 12 - 6 = 72$$~~

$$I_{1A} = I_A = 6A$$

$$I_{2A} = \frac{12}{3} = 4A$$

$$I_{3A} = \frac{12}{6} = 2A$$

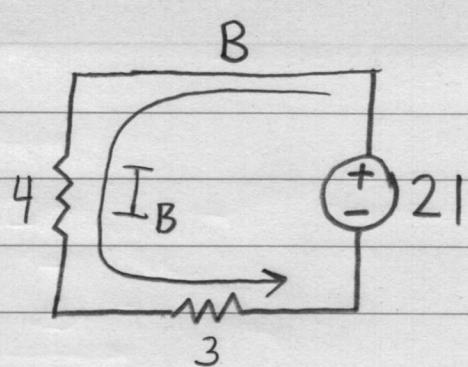

$$I_B = \frac{21}{4+3} = 3$$


$$V_b = 4 \cdot 3 = 12$$

~~$$V_d = 3 \cdot 3 = 9$$~~

$$I_{1B} = \frac{12}{12} = 1A$$

$$I_{2B} = I_B = 3A$$

$$I_{3B} = \frac{12}{6} = 2A$$




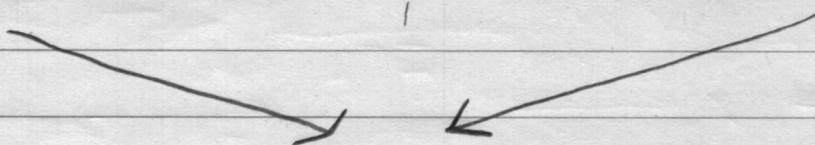



$$I_1 = I_{1A} - I_{1B} = 6 - 1 = 5A$$

$$I_2 = I_{2A} - I_{2B} = 4 - 3 = 1A$$

$$I_3 = I_{3A} + I_{3B} = 2 + 2 = 4A$$


Thevenin's Theorem

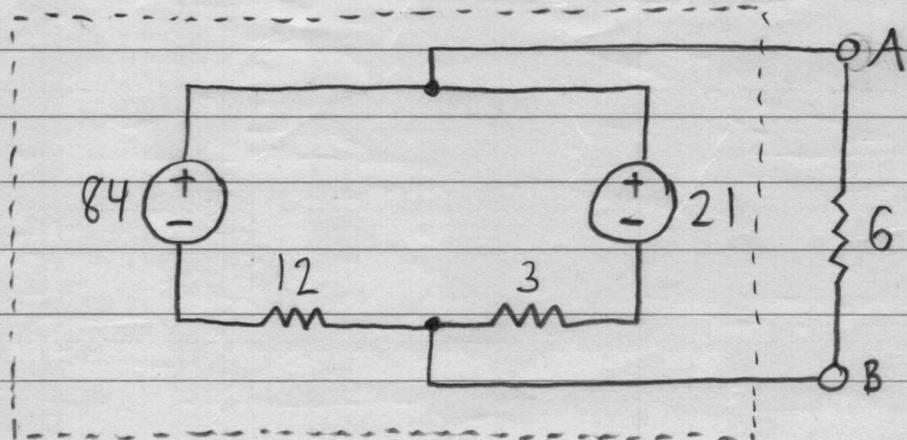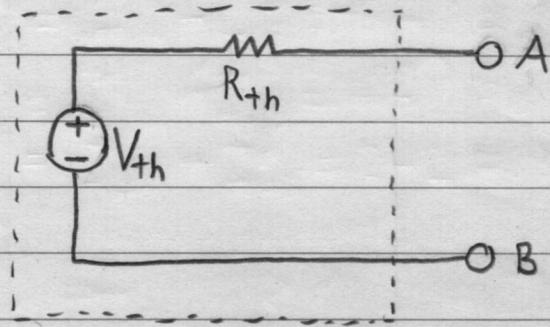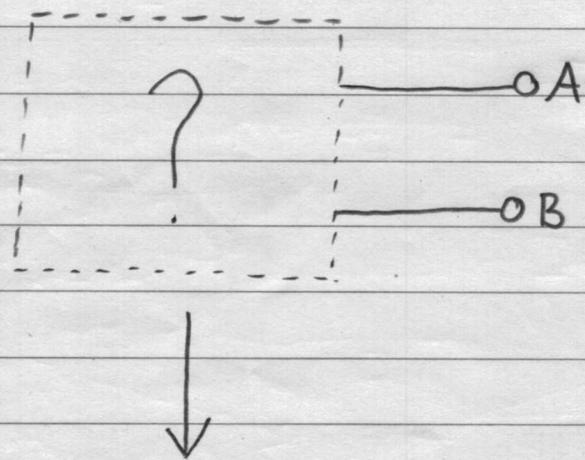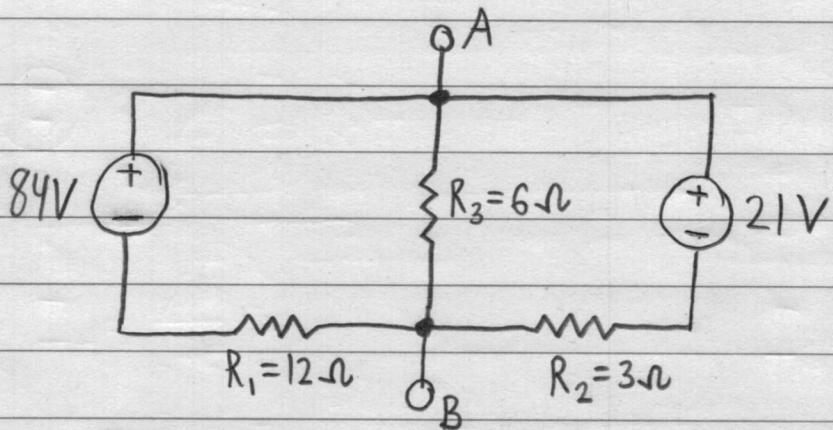

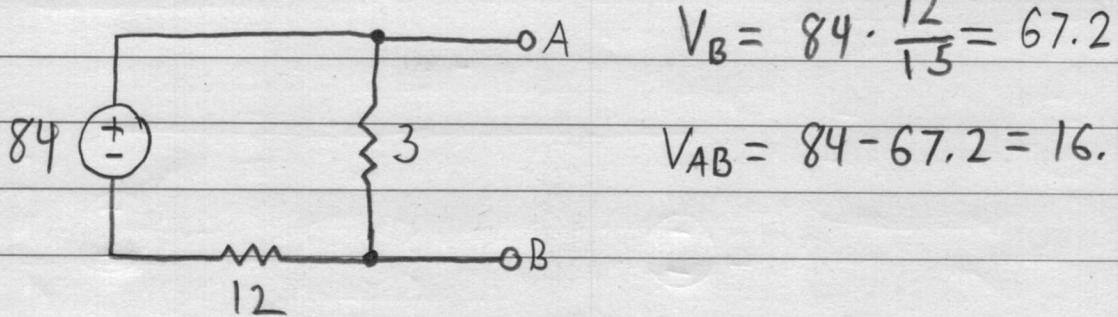

$$V_B = 84 \cdot \frac{12}{15} = 67.2$$


$$V_{AB} = 84 - 67.2 = 16.8V$$

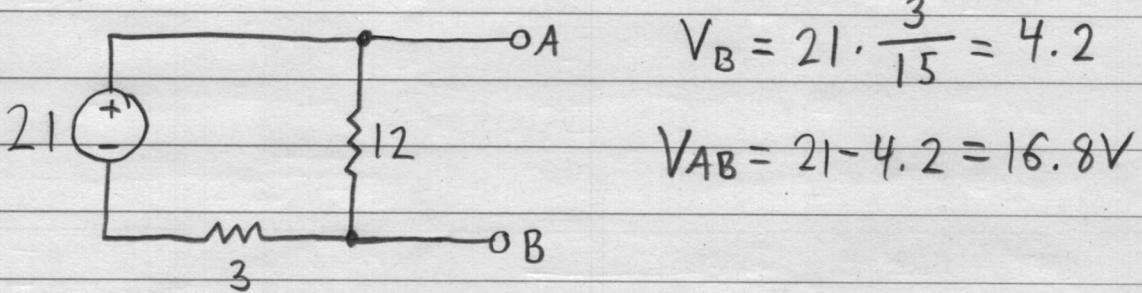

$$V_B = 21 \cdot \frac{3}{15} = 4.2$$



$$V_{AB} = 21 - 4.2 = 16.8V$$

$$V_{Th} = 16.8 + 16.8 = 33.6$$

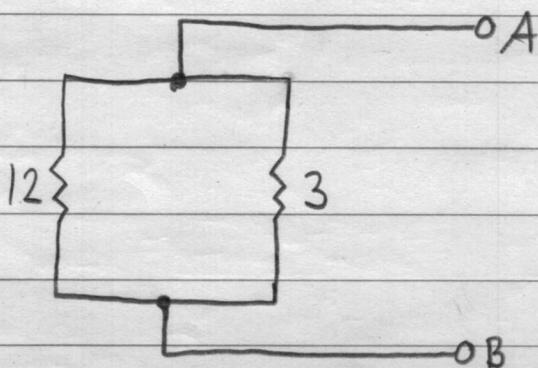


$$R_{Th} = 12 \parallel 3$$
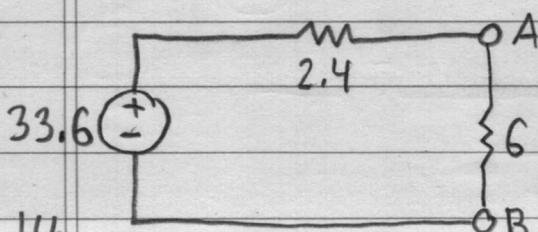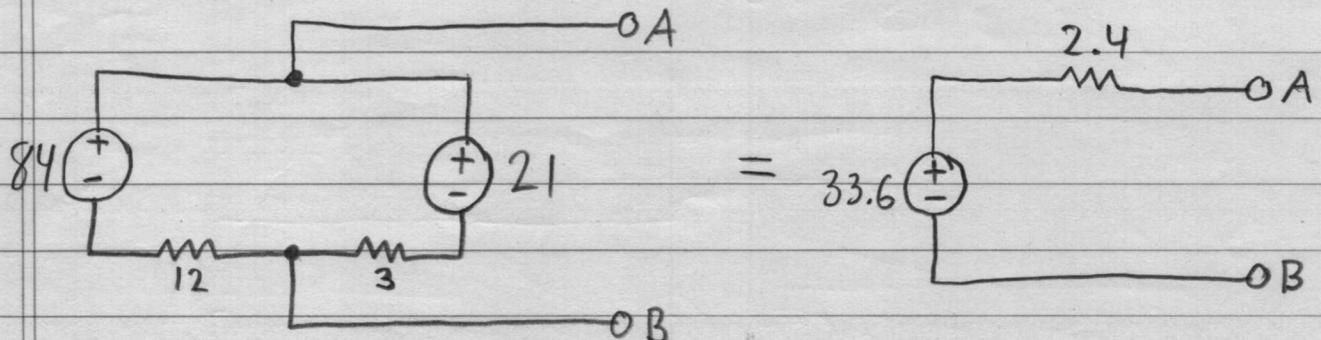
$$= \frac{12 \cdot 3}{12+3} = \frac{36}{15} = 2.4$$





$$V_{AB} = 33.6 \cdot \frac{6}{8.4} = 24V$$

Real Batteries

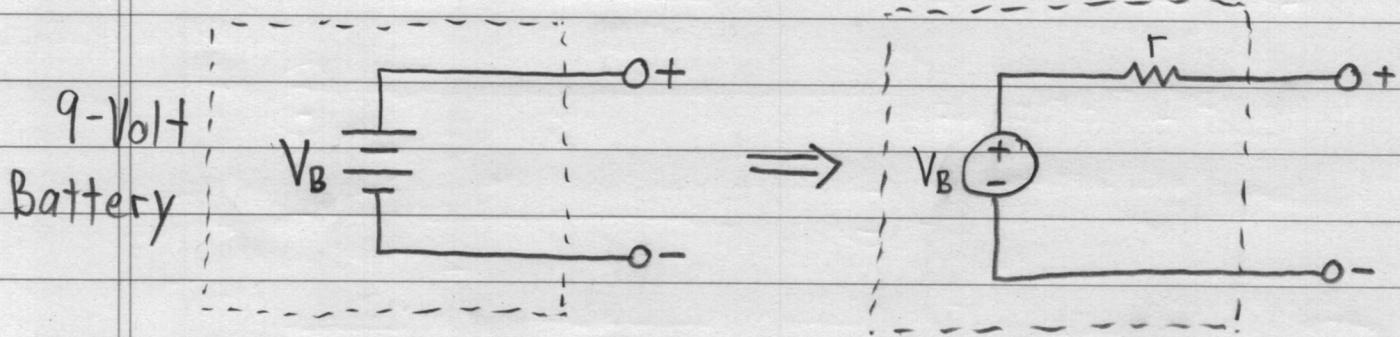

Measure and get $V_B = 9V$

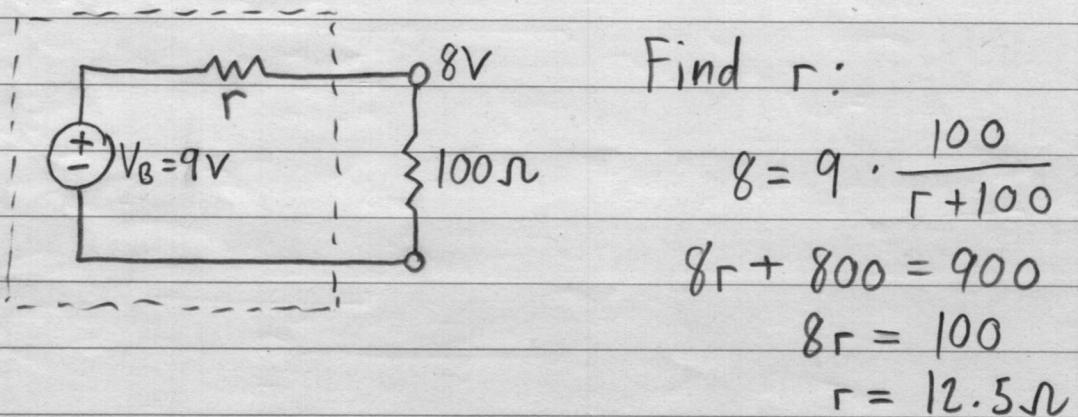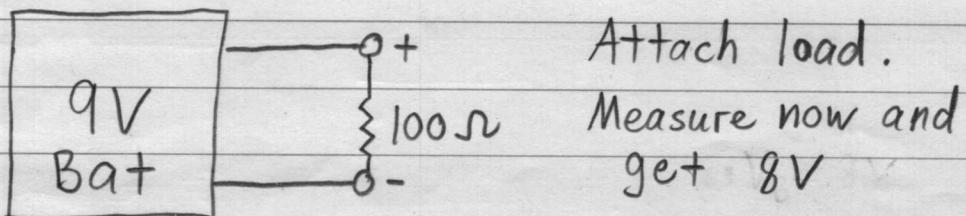

r is not constant. Weaker battery has a higher r . Heavier load results in higher r .

Diodes

Diodes are the basic semiconductor device

Semiconductor means that under certain conditions it will conduct and under other conditions it will not conduct (insulate).

Silicon is the most common.




Germanium used to be used frequently.

Gallium / Arsenic are used in light-emitting diodes (LEDs)
(4 valence electrons)

PN junction: Pure silicon is "doped" with impurities

p-type silicon: 3 valence electrons (Al)

n-type silicon: 5 valence electrons (P)

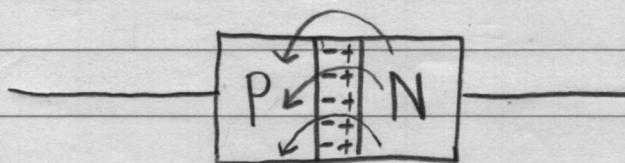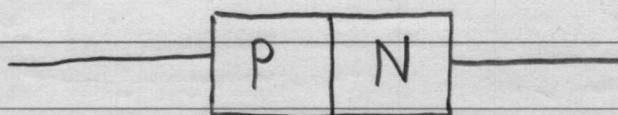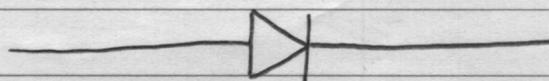



electrons jump over the depletion region

Diode equation: $I = I_o (e^{\frac{qV}{nKT}} - 1) \quad 1 \leq n \leq 2$


$$\frac{kT}{q} = V_T \quad @ 300K, V_T \approx 26mV \quad \therefore I = I_o (e^{\frac{V}{0.026n}} - 1)$$


Ideal Diode

Non-linear device

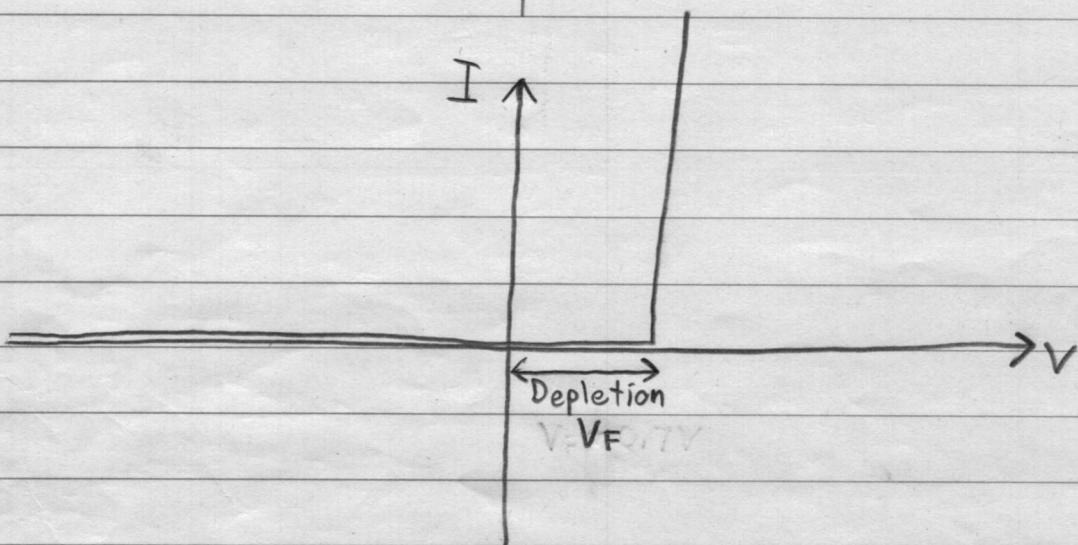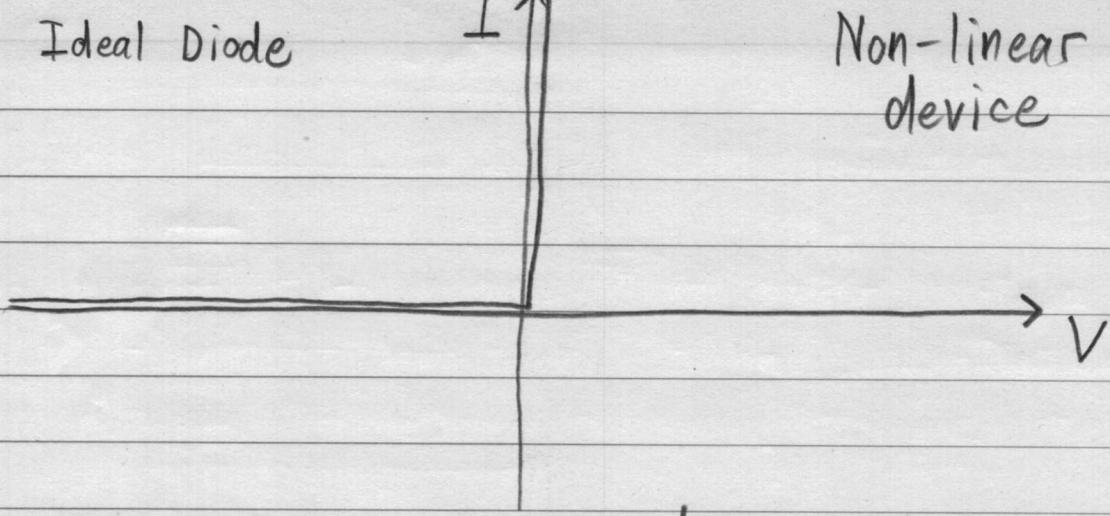


Silicon
Diode

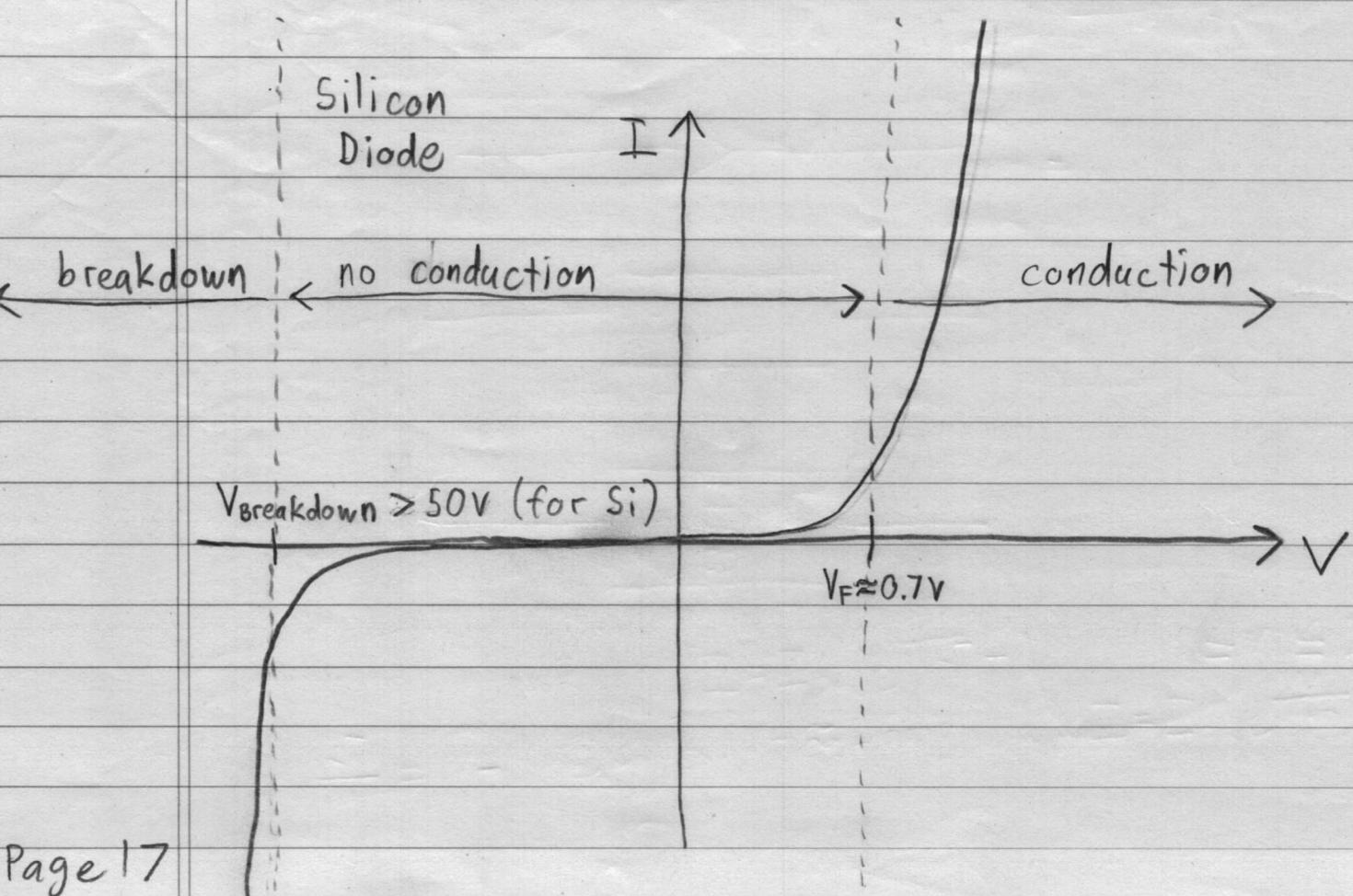

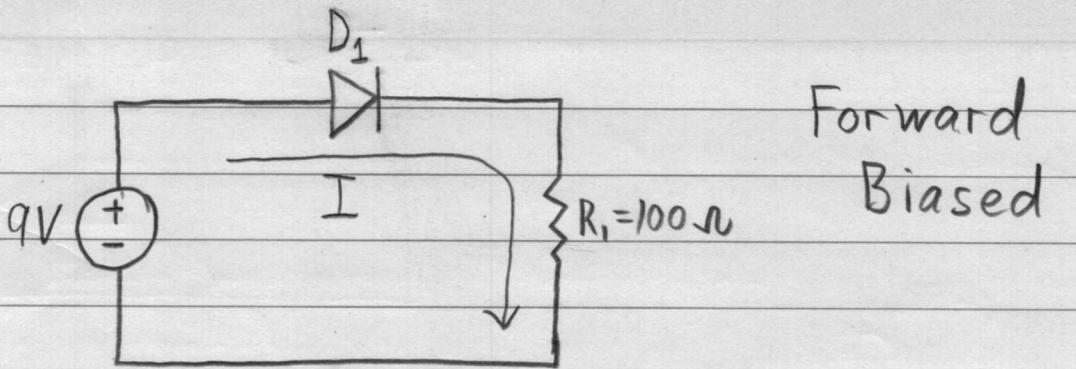


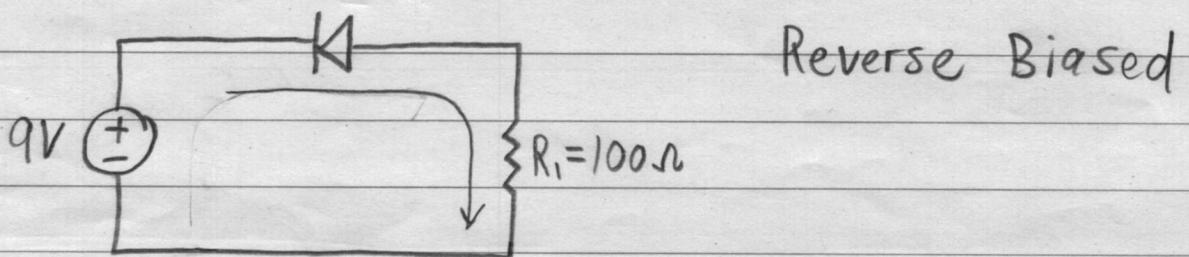
$$I = \frac{V_{RI}}{R_1} = \frac{9 - 0.7}{100} = \frac{8.3}{100} = 0.083A = 83mA$$



$$I = \frac{V_{RI}}{R_1} = \frac{0}{100} = 0A$$

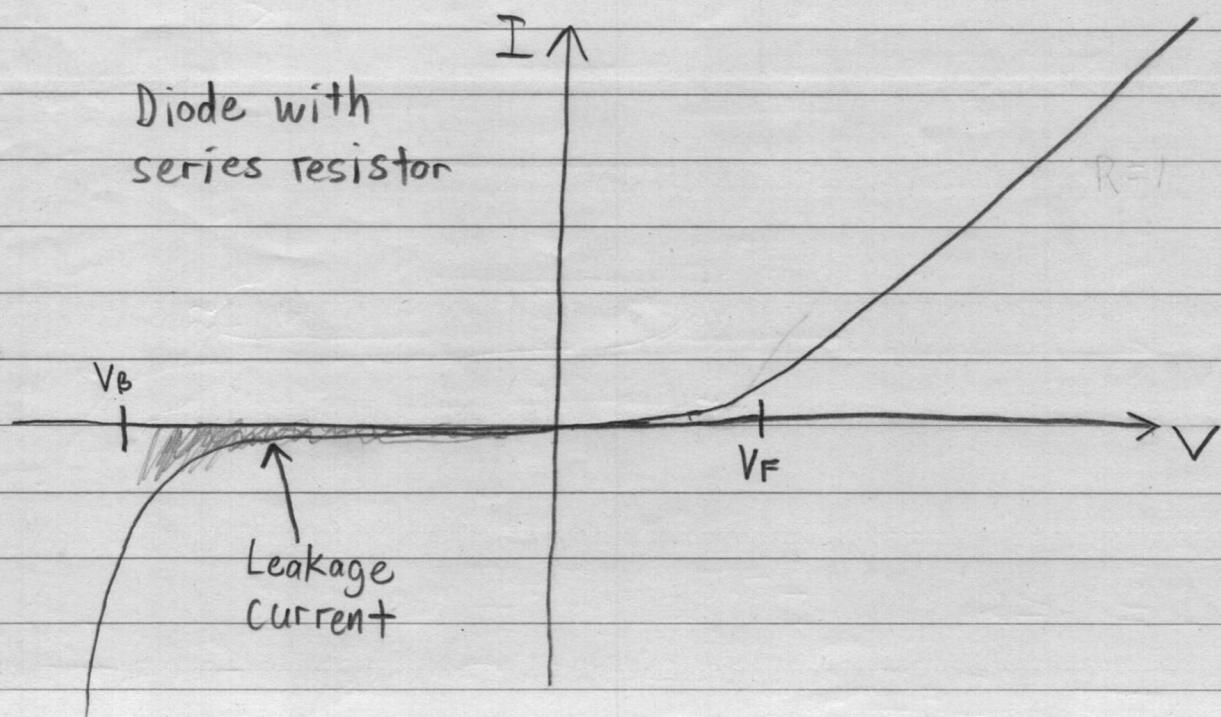Diodes have a spec called "leakage current" which is the small amount of current the diode conducts in reverse bias.



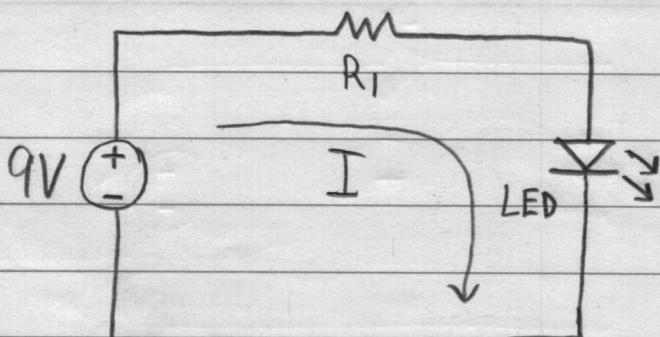

V_F for LEDs depends on the size and color. For basic red, green, and yellow LEDs: $V_F \approx 2.0V$ (see datasheet)

What should R_1 be such that 100mA flows through the LED ($I = 100mA$)

$$\text{KVL: } 9 - V_{R_1} - V_F = 0$$

$$9 - 2.0 = V_{R_1}$$

$$V_{R_1} = 7$$

$$I = \frac{V_{R_1}}{R_1}$$

$$0.1 = \frac{7}{R_1}$$

$$0.1R_1 = 7$$

$$R_1 = 70\Omega$$

LTspice

- 1.) Voltage Divider Circuit
- 2.) Analysis Circuit
- 3.) Thevenin Circuit
- 4.) Forward Diode Circuit
- 5.) Reverse Diode Circuit
- 6.) LED circuit